


ECE 270 (Spring 2022)

Homework 11-12

Due on 04/08/2022 (Friday) by 11:59 pm on BrightSpace.

 1. The following values are applied to S_L and R_L inputs of the NAND latch shown in the below figure in the same sequence indicated below.


$(S_L = 0, R_L = 1) \rightarrow (S_L = 0, R_L = 0) \rightarrow (S_L = 1, R_L = 1)$.



What is the corresponding stable Q , QN outputs for each of the input value sets in the above sequence?

 2. Sketch the outputs of a NOR based S-R latch for the input waveforms shown in the figure below.


Assume that input and output rise and fall times are zero, that the propagation delay of a NOR gate is 10 ns, and that each time division below is 10 ns.




3. A positive-edge-triggered J-K flip-flop has two control inputs J and K that control the device's behavior at the rising edge of CLK . If only J is asserted, the Q output is set to 1; if only K is asserted, Q is cleared to 0; if both are asserted, Q is toggled; and if neither is asserted, Q is not changed.

Show how to build a J-K flip-flop using a D flip-flop and combinational logic.

 4. A simple T flip-flop is given as shown below. If the input frequency of clock signal driving this flip-flop is 240 Hz and $T=1$ always, what is the frequency of the output signal Q ?



 5. In a digital circuit, if the set up-time margin is negative, then the circuit is said to have a set up time violation. Similarly, if the hold-time margin is negative, the circuit is said to have a hold time violation.




Consider the f_{in} (frequency) of the clock as 50 MHz. $T_{ffpd}(\min) = 1 \text{ ns}$, $T_{ffpd}(\max) = 2 \text{ ns}$, $T_{comb}(\min) = 0.5 \text{ ns}$, $T_{comb}(\max) = 1 \text{ ns}$, $T_{setup} = 2 \text{ ns}$, $T_{hold} = 1 \text{ ns}$.

Now, Please check if the above circuit has any set-up time or hold time violations with the given values of T_{ffpd} , T_{comb} , T_{setup} and T_{hold} values as above. If yes, provide the values of respective set up-time or hold time margins.

 6. A modulo- n counter counts the values from 0 to $n-1$ in the decimal system. For example, a modulo-4 counter can be used to count the values from 0 to 3.


The figure below shows a modulo- n binary counter which works on every positive clock edge. Find the value of ' n ' in this modulo- n counter ? (Assume Q_3, Q_2, Q_1, Q_0 are the outputs of your 4 flip flops which decodes as binary to decimal values upto $n-1$ with Q_3 as MSB and Q_0 as LSB)



7. Draw a 4-bit ring counter using D-Flipflops and give the output values of each flipflop for each clock cycle.

8. Implement a 3-bit ripple down counter using T-Flip Flop by showing the characteristic table and the final circuit diagram containing proper inputs/flipflops.

 9. Assuming all the flip-flops are in reset condition initially, what is the sequence observed at the output Q_A in the circuit shown for each clock cycle. Provide your answer for at least 6 clock cycles.



10. A 4-bit shift register, which shifts data right $Q_0 \rightarrow Q_1 \rightarrow Q_2 \rightarrow Q_3$, is shown in the below figure. The initial value for Q_0, Q_1, Q_2, Q_3 is 1000.

(a) Write the 4-bit values for Q_0, Q_1, Q_2 and Q_3 after each clock pulse until the pattern 1000 reappears.

(b) To what value should the shift register be initialized so that the pattern 1000 occurs after 2 clock pulses?

