

Homework 10

Solutions

1. $Q1^* = Q1' + Q2$

$$Q2^* = X.Q2'$$

$$Z = Q1 + Q2'$$

Q1	Q2	Q1*Q2*		Z	
		X = 0	X = 1	X=0	X=1
0	0	10	11	1	1
0	1	10	10	0	0
1	0	00	01	1	1
1	1	10	10	1	1

Present state	Input X = 0	Input X = 1
	Next state, Output	
A	C,1	D,1
B	C,0	C,0
C	A,1	B,1
D	C,1	C,1

2. Overlapping sequence 1001


State A - 3 or more 1s

State B - 1 or more consecutive 1s

State C - 10

State D - 100

Present state	Input X = 0	Input X = 1
	Next state, Output	
A	A, 0	B, 0
B	C, 0	B, 0
C	D, 0	B, 0
D	A, 0	B, 1

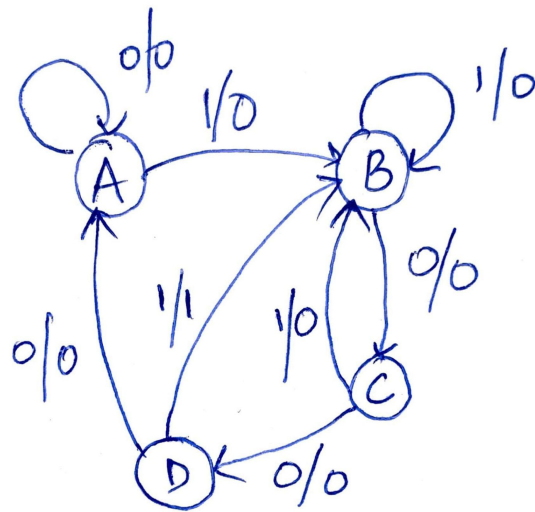


3. State A - 0101, 2 or more 1s

State B - 1 or more 0s

State C - 01


State D - 010

 

4. State A - 1 or more 1s

State B - 0

State C - 2 or more 0s

 

5.

Present state	Input X = 0	Input X = 1
	Next state, Output	
A	B, 0	C, 1
B	D, 0	F, 1

C	F,0	E,0
D	B,0	G,1
E	F,0	C,0
F	E,0	D,0
G	F,0	G,0

$P_0 = (ABCDEFG)$

To perform state minimization, we first separate the states based on the outputs for a 1 bit input.

For $X=0$, all outputs are same.

For $X=1$, outputs are 1 for ABD and 0 for CEF.

Hence, $P_1 = (ABD)(CEFG)$

P2:

$X=0 : ABD \Rightarrow BDB$

$CEFG \Rightarrow FFEF$

$X=1 : ABD \Rightarrow CFG$

$CEFG \Rightarrow ECDG$

Since ECG and D are in separate set of states, we can separate F from CEG

Thus $P_2 = (ABD)(CEG)(F)$

P3:

$X=0 : ABD \Rightarrow BDB$

$CEG \Rightarrow FFF$

$F \Rightarrow E$

$X=1 : ABD \Rightarrow CFG$

$CEG \Rightarrow ECG$

$F \Rightarrow D$

Since CG and F are in separate set of states, we can separate B from AD.

Thus $P3 = (AD)(B)(CEG)(F)$

P4:

$X=0 : AD \Rightarrow BB$

$B \Rightarrow D$

$CEG \Rightarrow FFF$

$F \Rightarrow E$

$X=1 : AD \Rightarrow CG$

$B \Rightarrow F$

$CEG \Rightarrow ECG$

$F \Rightarrow D$

$P4 = (AD)(B)(CEG)(F)$

Since $P3=P4$, no further separation can be done,

From $P4$, it is evident that A, D are equivalent states. And C,E,G are equivalent states.

We can therefore remove D,E,G from the state table.

Thus after minimization the state table looks like:

Present state	Input X = 0	Input X = 1
	Next state, Output	
A	B, 0	C, 1
B	A, 0	F, 1
C	F, 0	C, 0
F	C, 0	A, 0

6.

Present state	Input X = 0	Input X = 1
	Next state, Output	
A	A, 0	B, 0
B	C, 0	B, 0
C	D, 0	B, 0
D	A, 0	E, 0
E	C, 0	B, 1

State minimization:

P0 = (ABCDE)

P1:

X=0, all outputs are 0.

X=1, outputs are 0 for ABCD and 1 for E

P1 = (ABCD)(E)

P2:

X=0: ABCD => ACDA

E => C

X=1: ABCD => BBBE

E => B

P2 = (ABC)(D)(E)

P3:

X=0: ABC => ACD

D => A

E => C

X=1: ABC => BBB

D => E

$$E \Rightarrow B$$

$$P3 = (AB)(C)(D)(E)$$

P4:

$$X=0: AB \Rightarrow AC$$

$$C \Rightarrow D$$

$$D \Rightarrow A$$

$$E \Rightarrow C$$

$$X=1: AB \Rightarrow BB$$

$$C \Rightarrow B$$

$$D \Rightarrow E$$

$$E \Rightarrow B$$

$$P4 = (A)(B)(C)(D)(E)$$

No minimization is possible.

State assignment:

Present state Q0Q1Q2	Input X = 0	Input X = 1
	Next state, Output Q0*Q1*Q2*,Z	
000	000, 0	001,0
001	010,0	001,0
010	011,0	001,0
011	000,0	100,0
100	010,0	001,1

Q2X	00	01	11	10
Q0Q1 00				
01			1	
11	X	X	X	X

10			X	X
----	--	--	---	---

$$Q0^* = Q1Q2X$$

Q2X	00	01	11	10
Q0Q1 00				1
01	1			
11	X	X	X	X
10	1		X	X

$$Q1^* = Q1Q2'X' + Q1'Q2X' + Q0Q2'X'$$

Q2X	00	01	11	10
Q0Q1 00		1	1	
01	1	1		
11	X	X	X	X
10		1	X	X

$$Q2^* = Q2'X + Q1Q2' + Q0'Q1'X$$

Q2X	00	01	11	10
Q0Q1 00				
01				
11	X	X	X	X
10		1	X	X

$$Z = Q0X$$

7. .

Q0Q1Q2	Q0*Q1*Q2* D0D1D2	
	UP=1	UP=0
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110


8. Total no. of unique states required = $(70+5+75)/5 = 30$

No. of flip flops required = n

$$2^n \geq 30$$

Thus, n = 5

9.

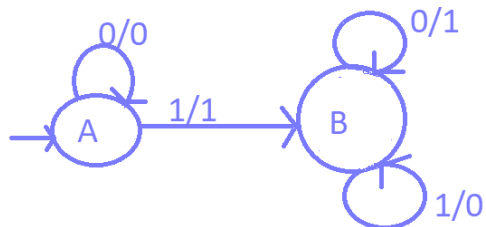

We know the regular method to find 2's complement. Another technique that is useful to draw a state machine is described below:

Start from the right. Do not change the no.s until you reach a 1. Leave the first 1 as such. Complement every no. to the left of the 1.

10. In Moore model the output depends only on the present state.

In Mealy model the output depends on both the present state and the inputs.

```
module FSM(CLOCK,XZ);  
input CLOCK,X;  
output reg Z;  
reg [2:0] Sreg,Snext;  
parameter [2:0] S0=3'b000,
```

```
S1=3'b001,  
S2=3'b010,  
S3=3'b011
```

```
/* create state memory  
always @(posedge CLOCK)
```

```
Sreg <= Snext;
```

```
/* create next-state logic */
```

```
always @(X,Sreg)  
begin  
case(Sreg)  
S0: if(X==0) Snext=S0;  
else Snext=S1;  
S1: if(X==0) Snext=S2;  
else Snext=S0;  
S2: if(X==0) Snext=S3;  
else Snext=S2;  
S3: if(X==0) Snext=S1;  
Snext=S0;  
default: Snext=S0;  
endcase  
end
```

```
/* create output logic */  
always @(Sreg)  
case(Sreg)  
S0,S1,S2: Z=0;  
S3: Z=1;  
default: Z=0;  
endcase  
endmodule
```