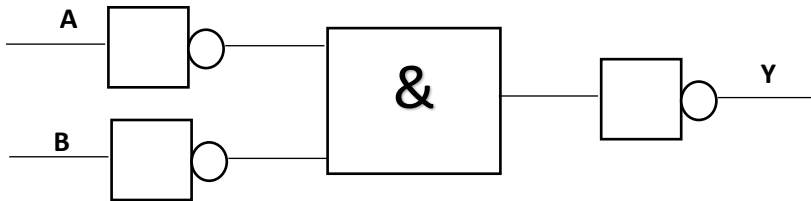


## PRACTICE1 – SOLUTIONS


1)





A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

An OR circuit gives the same output behavior, that is,  $Y = A + B$ .


2)

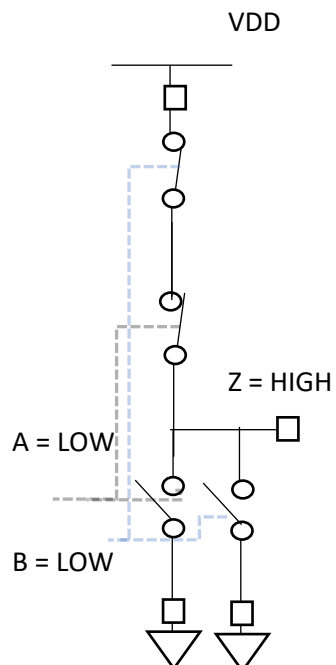

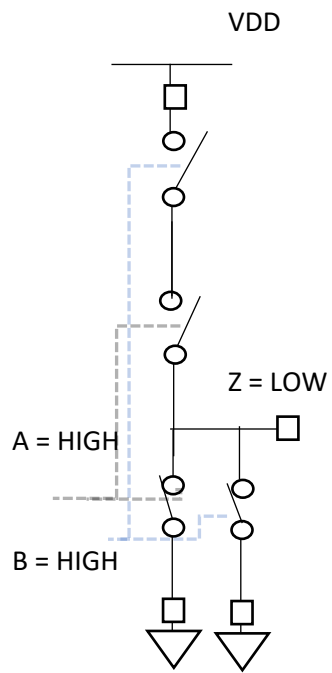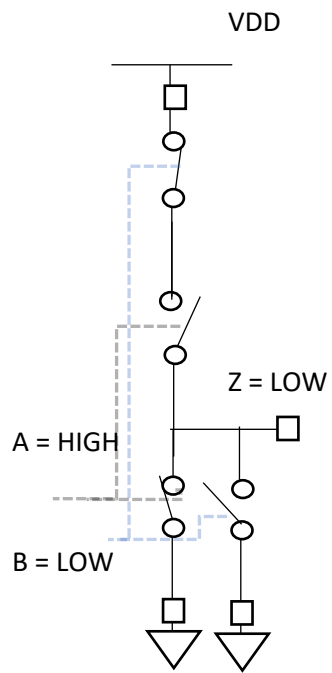


3)

**Figure 1-19**  
Multiplexer design  
using CMOS  
transmission gates.

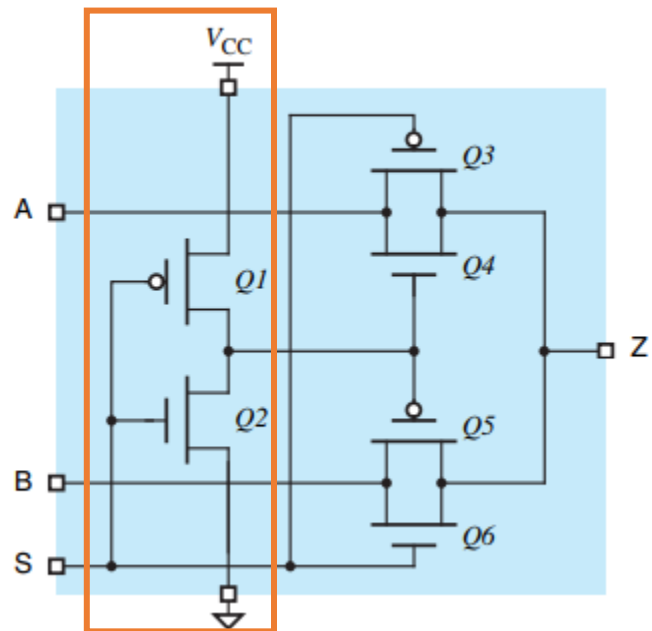



The part of the circuit highlighted with the orange box acts as an inverter. Hence, transistors Q1, Q2 form an inverter.

4)

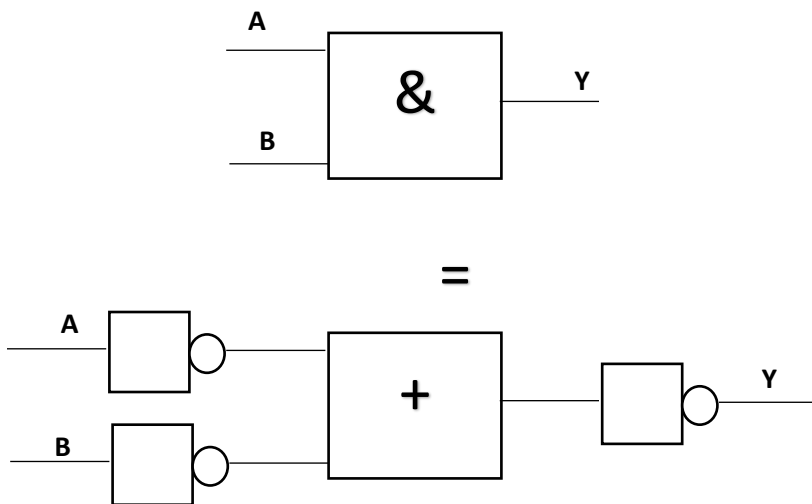

$$Y = A \cdot B = (A' + B')'$$

5)

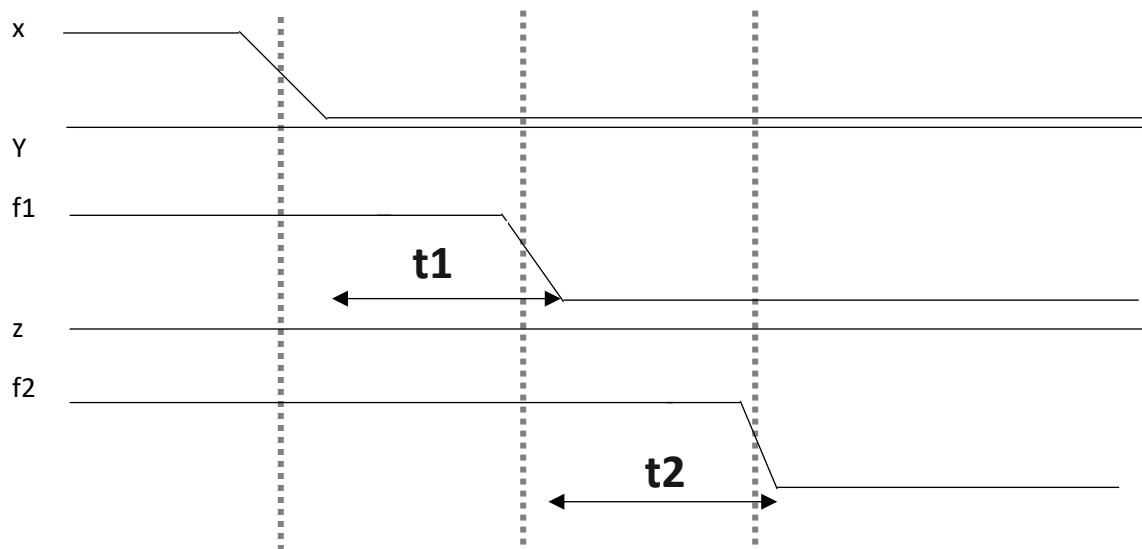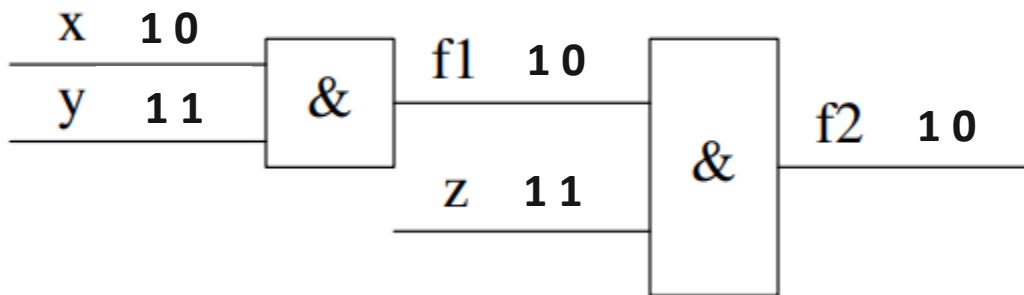

t1: propagation delay from x to f1

t1: propagation delay from f1 to f2

6)

