

Homework 4 Solutions


$$1. F = X'Y'Z + X'YZ + Y'X + Y'Z$$

$$= X'Z(Y' + Y) + Y'X + Y'Z$$

$$= X'Z + XY' + Y'Z$$

$$= X'Z + XY'$$

Implementation:

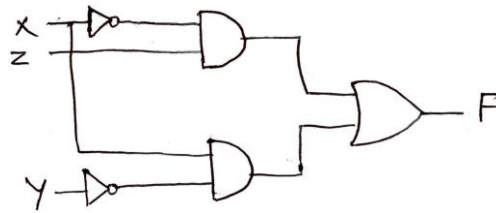

2. Proof can be obtained by solving as below:

$$\begin{aligned} F1 &= (X + Y) \cdot (Y' + Z) \cdot (X' + Z') \\ &= (X + Y + (Z \cdot Z')) \cdot ((X \cdot X') + Y' + Z) \cdot (X' + (Y \cdot Y') + Z') \\ &= ((X + Y + Z) \cdot (X + Y + Z')) \cdot ((X' + Y' + Z) (X + Y' + Z)) \cdot ((X' + Y + Z') \cdot (X' + Y + Z')) \\ &= \pi(0,1,2,6,5,7) \end{aligned}$$

$$\begin{aligned} F2 &= (X + Z) \cdot (X' + Y') \cdot (Y + Z') \\ &= (X + (Y \cdot Y') + Z) \cdot (X' + Y' + (Z \cdot Z')) \cdot ((X \cdot X') + Y + Z') \\ &= ((X + Y + Z) \cdot (X + Y' + Z')) \cdot ((X' + Y' + Z) (X' + Y' + Z')) \cdot ((X + Y + Z') \cdot (X' + Y + Z')) \\ &= \pi(0,2,6,7,1,5) \end{aligned}$$


$$F1 = F2$$

Hence Proved.

3. The canonical sum of a function is the sum of all minterms that produce a value of 1. If those minterms cannot be grouped in any manner in the K-map, then the minimal sum is the canonical sum. The no. of literals in the product term of such a function is n since canonical sums always have n literals.

Ex: Even parity detector function.


4. K-Map can be drawn as below:

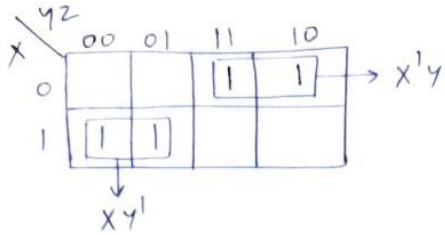

$XY'$  and  $X'Y$  are the prime implicants

So, minimal sum =  $XY' + X'Y$

5. K-Map can be drawn as below:

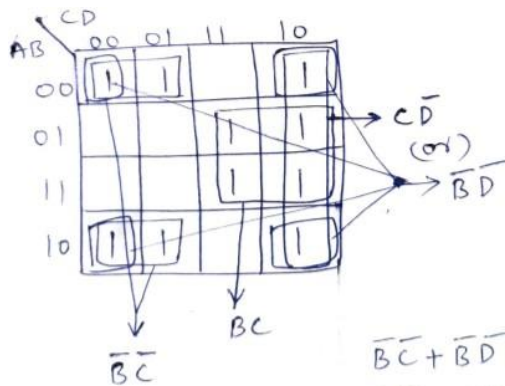


$\overline{B}\overline{C} + \overline{B}\overline{D} + BC$  (or)

So, minimal sum =  $\overline{B}\overline{C} + \overline{C}\overline{D} + BC$

Essential prime implicants =  $\{BC, \overline{B}\overline{C}, \overline{C}\overline{D}\}$

(or)  
 $\{BC, \overline{B}\overline{C}, \overline{B}\overline{D}\}$

6. K-Map can be drawn as below:

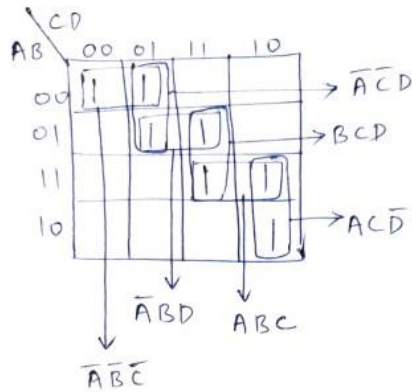


So, above 6 terms are the Prime implicants

→ Essential prime implicants

$$= A\bar{C}\bar{D}, \bar{A}\bar{B}\bar{C}$$

7. K-Map can be drawn as below:

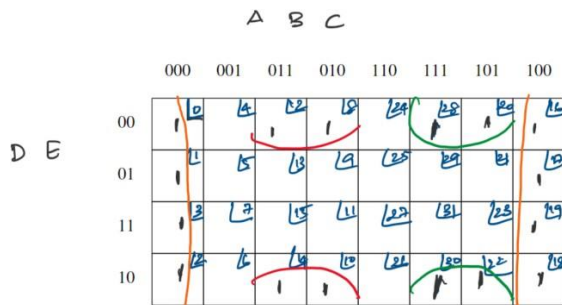

$$F(A, B, C, D, E) = \sum (0, 1, 2, 3, 8, 9, 10, 11, 14, 15, 16, 17, 18, 19, 20, 23, 28, 30)$$

$$= \bar{B}\bar{C} + \bar{A}\bar{B}\bar{E} + A\bar{C}\bar{E}$$

#### FINDING PRIME IMPLICANTS USING QUINE McCLUSKEY METHOD

Group Decimal Binary

0 0 00000

1 1 00001

1 2 00010

1 8 01000

1	16	10000
2	3	00011
2	10	01010
2	12	01100
2	17	10001
2	18	10010
2	20	10100
3	14	01110
3	19	10011
3	22	10110
3	28	11100
4	30	11110

Group    Decimal    Binary

0	0, 16	-0000
0	0, 8	0-000
0	0, 2	000-0
0	0, 1	0000-
1	1, 17	-0001
1	1, 3	000-1
1	18, 2	-0010
1	10, 2	0-010
1	2, 3	0001-
1	12, 8	01-00

1	10, 8	010-0
1	16, 20	10-00
1	16, 18	100-0
1	16, 17	1000-
2	19, 3	-0011
2	10, 14	01-10
2	12, 28	-1100
2	12, 14	011-0
2	17, 19	100-1
2	18, 22	10-10
2	18, 19	1001-
2	20, 28	1-100
2	20, 22	101-0
3	14, 30	-1110
3	22, 30	1-110
3	28, 30	111-0

Group	Decimal	Binary
0	0, 16, 18, 2	-00-0
0	0, 1, 16, 17	-000-
0	0, 10, 2, 8	0-0-0 ✱
0	0, 1, 2, 3	000--
1	1, 17, 19, 3	-00-1
1	18, 19, 2, 3	-001-

1      10, 12, 14, 8    01--0 \*

1      16, 18, 20, 22    10--0 \*

1      16, 17, 18, 19    100--

2      12, 14, 28, 30    -11-0 \*

2      20, 22, 28, 30    1-1-0 \*

Group    Decimal                      Binary

0          0, 1, 16, 17, 18, 19, 2, 3   -00-- \*

**Prime Implicants:  $A'C'E'$ ,  $A'BE'$ ,  $AB'E'$ ,  $BCE'$ ,  $ACE'$ ,  $B'C'$**

8. A prime number detector provides an output of 1 if the inputs correspond to a prime no.

Eg: If  $N_1N_2N_3N_4$  is 0010, then output F is 1 since, 2 is a prime number.

K-Map can be drawn and simplified as below.


		$N_3N_2$			
		00	01	11	10
$N_1N_0$	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

$$F = N_2\bar{N}_1N_0 + \bar{N}_2N_1N_0 + \bar{N}_3N_1N_0 + \bar{N}_3\bar{N}_2N_1$$

9.  $F = \Pi_{ABCD}(1,3,6,7,9,15,14)$

In other words,


$$F' = \sum_{ABCD}(1,3,6,7,9,15,14)$$

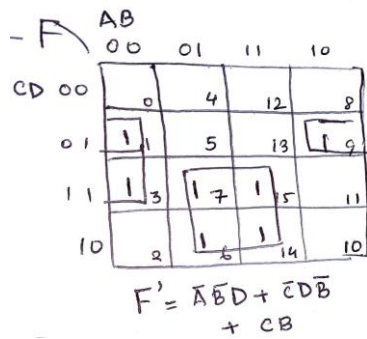

Hence, Simplified solution is

$$F = F'' = (A'B'D + C'DB' + CB)' = (A+B+D')(C+D'+B)(C'+B')$$

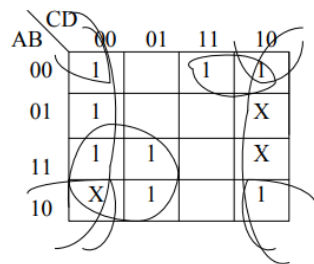10. The K-Map can be drawn as below. Don't cares are denoted by 'X'.



The prime implicants are :  $D'$ ,  $B'D'$ ,  $AC'$ ,  $A'B'C$   
 The essential prime implicants are :  $D'$ ,  $AC'$ ,  $A'B'C$   
 The simplified expression is :  $Y = D' + AC' + A'B'C$