 



## HOMEWORK 6

### SOLUTIONS

- Since both the NMOS and PMOS transistors have some resistance associated with them under ON conditions, a resistive load changes the output voltage due to voltage divider action. For a LOW input voltage, the output voltage is lower than the actual output HIGH (5V). For a HIGH input voltage, the output voltage is higher than the actual output LOW (0V).





When PMOS is ON ( $V_{in} = 0V$ )

 

When NMOS is ON ( $V_{in} = 5V$ )

  - $I_{OHMAX}$  is the maximum current that the output can source when it is HIGH while still maintaining an output voltage no lesser than  $V_{OHmin}$ . For the output to be high the PMOS has to be turned ON. The NMOS is OFF and thus has very high resistance.



$$V_{OUT} = \frac{3K}{3100\Omega} \times 5V$$



$$\Rightarrow \frac{30 \times 5}{31}$$

$$\Rightarrow 4.83V$$

$$I_{OHMAX} = \frac{(5 - 4.83)V}{100\Omega}$$

$$= 1.7mA$$

3.

 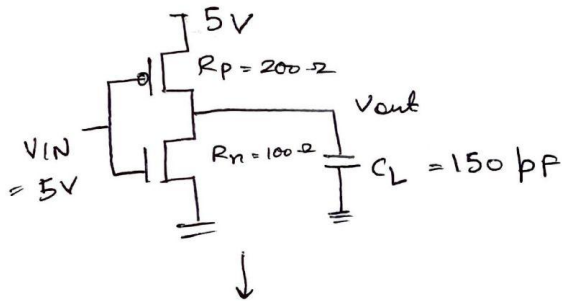

By Kirchhoff's voltage law.

$$\frac{d}{dt}(C V_{out}) = -\frac{V_{out}}{R}$$

$$\Rightarrow C \frac{dV_{out}}{dt} = -\frac{V_{out}}{R}$$

$$\Rightarrow RC \frac{dV_{out}}{V_{out}} = -dt$$

$$\Rightarrow \int_{0.2V_{DD}}^{0.8V_{DD}} \frac{dV_{out}}{V_{out}} = -\int_0^{t_{fall}} \frac{dt}{RC}$$

$$= \int_{0.2V_{DD}}^{0.8V_{DD}} \frac{dV_{out}}{V_{out}} = \int_0^{t_{fall}} \frac{dt}{RC}$$

$$\Rightarrow \ln 4 = \frac{t_{fall}}{RC}$$

$$\Rightarrow t_{fall} = 100 \times 150 \times 10^{-12} \times \ln 4$$

$$= 20.8 \text{ ns}$$

4. i) Dissipation due to direct current path - This happens when the input voltage undergoes a transition and both the PMOS and NMOS transistors are ON for a short interval of time as the input voltage is not close to 0V or Vdd.

$$P_T = C_{PD} * V_{dd}^2 * f$$


where  $f$  is the transition frequency and  $C_{PD}$  is a constant that represents the physical effects that occur in the device.

ii) Dissipation due to capacitive load at the output - The energy dissipated due to charging and discharging of the output capacitor, which can be a combination of internal capacitance, interconnect capacitance, and external load capacitance.

$$P_L = C_L * V_{dd}^2 * f$$

Where  $f$  is the transition frequency and  $C_L$  is the load capacitance.

 5. The high-impedance output state is created by turning off both the PMOS and NMOS transistors using the EN signal.



6. We can connect tri-state buffers at the output of each device before connecting to the bus. A decoder logic can be used to set the enable signals of the tri-state buffers thus ensuring that only one device is accessing the bus at a time. The outputs of all the other devices are held in a high-impedance (Z) state.
7. 

```
module Mux21 (A,B,S,Y) ;  
    output Y;  
    input A, B, S;  
    assign Y = S?B:A; (or Y = S?A:B)  
endmodule
```
8.  $Y = 5'b0X011$
9.  $3*4+6+4 = 22$
10. 

```
reg [31:0] A [0:127]  
assign B = A[5]
```