

ECE 270 (Spring 2022)

Homework 3 Solutions

Due on 02/04/2022 (Friday) by 11:59 pm sharp on BrightSpace.

1. As per consensus theorem:

$$XY + X'Z + YZ = XY + X'Z$$

$$\begin{aligned} &XY + X'Z + YZ \\ \Rightarrow &XY + X'Z + YZ(X+X') \\ \Rightarrow &XY + XYZ + X'Z + YZX' \\ \Rightarrow &XY(1+Z) + X'Z(1+Y) \\ \Rightarrow &XY + X'Z \end{aligned}$$

$$(X+Y) \cdot (X'+Z) \cdot (Y+Z) = (X+Y) \cdot (X'+Z)$$

$$\begin{aligned} &(X+Y) \cdot (X'+Z) \cdot (Y+Z) \\ \Rightarrow &(X+Y) \cdot (X'+Z) \cdot (Y+Z+(X \cdot X')) \\ \Rightarrow &(X+Y) \cdot (X+Y+Z) \cdot (X'+Z) \cdot (X'+Z+Y) \\ \Rightarrow &(X+Y) \cdot (X'+Z) \end{aligned}$$

2. 000, 011, 010, 001. To reduce the error, we can use gray code instead of binary-coded values since there is only one bit change between two consecutive gray code numbers.
3. Let $a_1, a_2, a_3, \dots, a_n$ be the inputs and b be the output of an n -input OR gate.

$$\begin{aligned} &\text{Therefore, } a_1 + a_2 + a_3 + \dots + a_n = b \\ \Rightarrow &((((a_1 + a_2) + a_3) + a_4) + \dots + a_n) = b \end{aligned}$$

If a_1, a_2 are inputs to the first 2-input OR gate. Its output and a_3 are inputs to the 2nd OR-gate, and so on.

Hence an n -input OR gate can be replaced by $n-1$ 2-input OR gates.

There are other ways to implement the same.

$$\text{Eg: } ((a_1 + a_2) + (a_3 + a_4)) + ((a_5 + a_6 + \dots)) = b$$

Any suitable implementation with proper justification is fine.

4. $F = (A + B) \cdot (B + C) \cdot (C + A)$
 $= (A \cdot B + B \cdot B + A \cdot C + B \cdot C) \cdot (C + A)$ (using Distributive law)

$$= (A.B.C + B.C + A.C + B.C + A.B + A.B + A.C + A.B.C) \text{ (using Distributive law)}$$

$$= (A.B.C + B.C + A.C + A.B) \text{ (combining terms)}$$

$$= (B.C + A.C + A.B) \text{ (combining terms)}$$

$$= F^D$$

Hence, F is a self- dual logic function

5.

$$F = (X' . Y) + (X + Y')$$

$$F' = ((X' . Y) + (X + Y'))'$$

$$= (X' . Y)' . (X + Y)'$$

$$= (X + Y') . (X' . Y)$$

6.

$$\text{LHS} = W . (X' + Y') + X' . (X' + Y') . (W' + X . Z)$$

$$= (W . X' + W . Y' + X' . X' + X' . Y') . (W' + X . Z) \text{ ---- (using Distributive law)}$$

$$= (W . X' + W . Y' + X' + X' . Y') . (W' + X . Z) \text{ ---- } (X' . X' = X')$$

$$= (W . X' + W . Y' + X') . (W' + X . Z) \text{ --- } (X' . Y' + X' = X')$$

$$= (W . Y' + X') . (W' + X . Z) \text{ --- } (W . X' + X' = X')$$

$$= (W . Y' . W' + X' . W' + W . X . Y' . Z + X' . X . Z) \text{ ---- (using Distributive law)}$$

$$= W . X . Y' . Z + W' . X' \text{ ---- } (X' . X . Z = W . Y' . W' = 0)$$

7. $2^8 = 256$ – since there are 8 rows in truth table with 3 variables, and each row has two options for output value.

8. Truth Table:

P	T	Z	T'	PT'	P+Z	PT'(P+Z)
0	0	0	1	0	0	0
0	0	1	1	0	1	0
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	0	0	1	0
1	1	1	0	0	1	0

$$9. \text{ Canonical Sum} = \sum(4,5) = PT'Z' + PT'Z$$

$$\text{Canonical Product} = \pi(0,1,2,3,6,7)$$

This can also be written as $(P+T+Z).(P+T+Z').(P+T'+Z).(P+T'+Z').(P'+T'+Z).(P'+T'+Z')$

10. $Y = \Pi (2,3,6,8,10,11,13,14,15)$ – List of all maxterms corresponding to the truth table rows where the function is 0.