 


**ECE 270 (Spring 2022)**

**Homework 6**


**Due on 02/25/2022 (Friday) by 11:59 pm on BrightSpace.**

1. Explain the effects of a resistive load on the output voltage of a CMOS inverter.
2. Determine the  $I_{OHMAX}$  and  $V_{OUT}$  in the following circuit.  $R_p$  is the ON-state resistance of the PMOS and whereas  $R_n$  is the OFF-state resistance of the NMOS transistor.




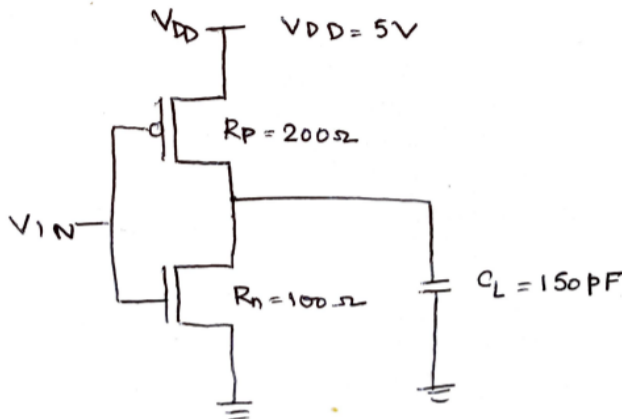3. If fall time is defined as the time taken by the output voltage to go from 80% of the maximum value to 20%, then what is the fall time for the following inverter circuit considering a capacitive load?  $R_p$  and  $R_n$  are the ON-state resistance of the PMOS and NMOS transistors respectively.

Hint: Use the formula  $V_{OUT} = V_{DD} \cdot e^{-t/(R_n C_L)}$



 4. What are the two components of dynamic power in a CMOS circuit?
5. Shown below is a tri-state inverter and its functionality. How can we create a tri-state inverter device using CMOS transistors? Explain with a circuit diagram.



EN	OUT
1	Z
0	IN'

6. Consider multiple devices connected to the same bus. How can we ensure that only one device accesses the bus at a time? Explain.
7. Using the conditional operator, write a simple behavioral Verilog code for a 2:1 multiplexer circuit.
8. What is the value of Y in the following Verilog code:

```

A = 5'b0X011;
if (A === 3'b0X1)
    Y = (A << 2) | 01001;
else
    Y = A;

```

9. Based on the below Verilog statements, how many bits are there in the variable Y?

```

Reg [15:0] A;
Reg [3:0] B;
Y = {3{B}, A[13:8], 4'b0};

```

10. Write the Verilog syntax to declare an array A of 128 32-bit vectors. Assign the 5th element of the array to a register B.